

### Exercise 1.1

(a)  $R = 5\text{k} + 10\text{k} = \boxed{15\text{k}\Omega}$

(b)  $R = \frac{R_1 R_2}{R_1 + R_2} = \frac{5\text{k} \cdot 10\text{k}}{5\text{k} + 10\text{k}} = \boxed{3.33\text{k}\Omega}$

### Exercise 1.2

$$P = IV = \left(\frac{V}{R}\right) V = \frac{(12\text{V})^2}{1\Omega} = \boxed{144\text{W}}$$

### Exercise 1.3

**TODO: Solve this problem**

### Exercise 1.4

**TODO: Solve this problem**

### Exercise 1.5

Given that  $P = \frac{V^2}{R}$ , we know that the maximum voltage we can achieve is 15V and the smallest resistance we can have across the resistor in question is 1k $\Omega$ . Therefore, the maximum amount of power dissipated can be given by

$$P = \frac{V^2}{R} = \frac{(15\text{V})^2}{1\text{k}\Omega} = \boxed{0.225\text{W}}$$

This is less than the 1/4W power rating.

### Exercise 1.10


(a) With two equal-value resistors, the output voltage is half the input voltage.

$$V_{out} = \frac{1}{2}V_{in} = \frac{30\text{V}}{2} = \boxed{15\text{V}}$$

(b) To treat  $R_2$  and  $R_{load}$  as a single resistor, combine the two resistors which are in parallel to find that the combined (equivalent) resistance is 5k $\Omega$ . Now, we have a simple voltage divider with a 10k $\Omega$  resistor in series with the 5k $\Omega$  equivalent resistor. The output voltage is across this equivalent resistance. The output voltage is given by

$$V_{out} = V_{in} \frac{5\text{k}\Omega}{10\text{k}\Omega + 5\text{k}\Omega} = \frac{30\text{V}}{3} = 10\text{V}$$

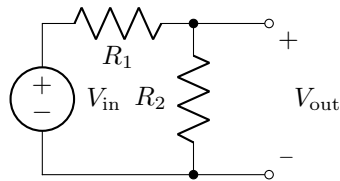- (c) We can redraw the voltage divider circuit to make the “port” clearer.



We can find  $V_{Th}$  by leaving the ports open (open circuit) and measuring  $V_{out}$ , the voltage across  $R_2$ . This comes out to be half the input voltage when  $R_1 = R_2$ , so  $V_{out} = 15V$ . Thus  $V_{Th} = 15V$ .

To find the Thévenin resistance, we need to find the short circuit current,  $I_{SC}$ .

**TODO: finish**

